

---

# Memory System Design

Chapter 16  
S. Dandamudi

---

# Outline

---

- Introduction
  - A simple memory block
    - \* Memory design with D flip flops
    - \* Problems with the design
  - Techniques to connect to a bus
    - \* Using multiplexers
    - \* Using open collector outputs
    - \* Using tri-state buffers
  - Building a memory block
- Building larger memories
  - Mapping memory
    - \* Full mapping
    - \* Partial mapping
  - Alignment of data
  - Interleaved memories
    - \* Synchronized access organization
    - \* Independent access organization
    - \* Number of banks

# Introduction

---


- To store a single bit, we can use
  - \* Flip flops or latches
- Larger memories can be built by
  - \* Using a 2D array of these 1-bit devices
    - » “Horizontal” expansion to increase word size
    - » “Vertical” expansion to increase number of words
- Dynamic RAMs use a tiny capacitor to store a bit
- Design concepts are mostly independent of the actual technique used to store a bit of data

# Memory Design with D Flip Flops

---

- An example
  - \* 4X3 memory design
  - \* Uses 12 D flip flops in a 2D array
  - \* Uses a 2-to-4 decoder to select a row (i.e. a word)
  - \* Multiplexers are used to gate the appropriate output
  - \* A single WRITE (WR) is used to serve as a write and read signal
    - zero is used to indicate write operation
    - one is used for read operation
  - \* Two address lines are needed to select one of four words of 3 bits each

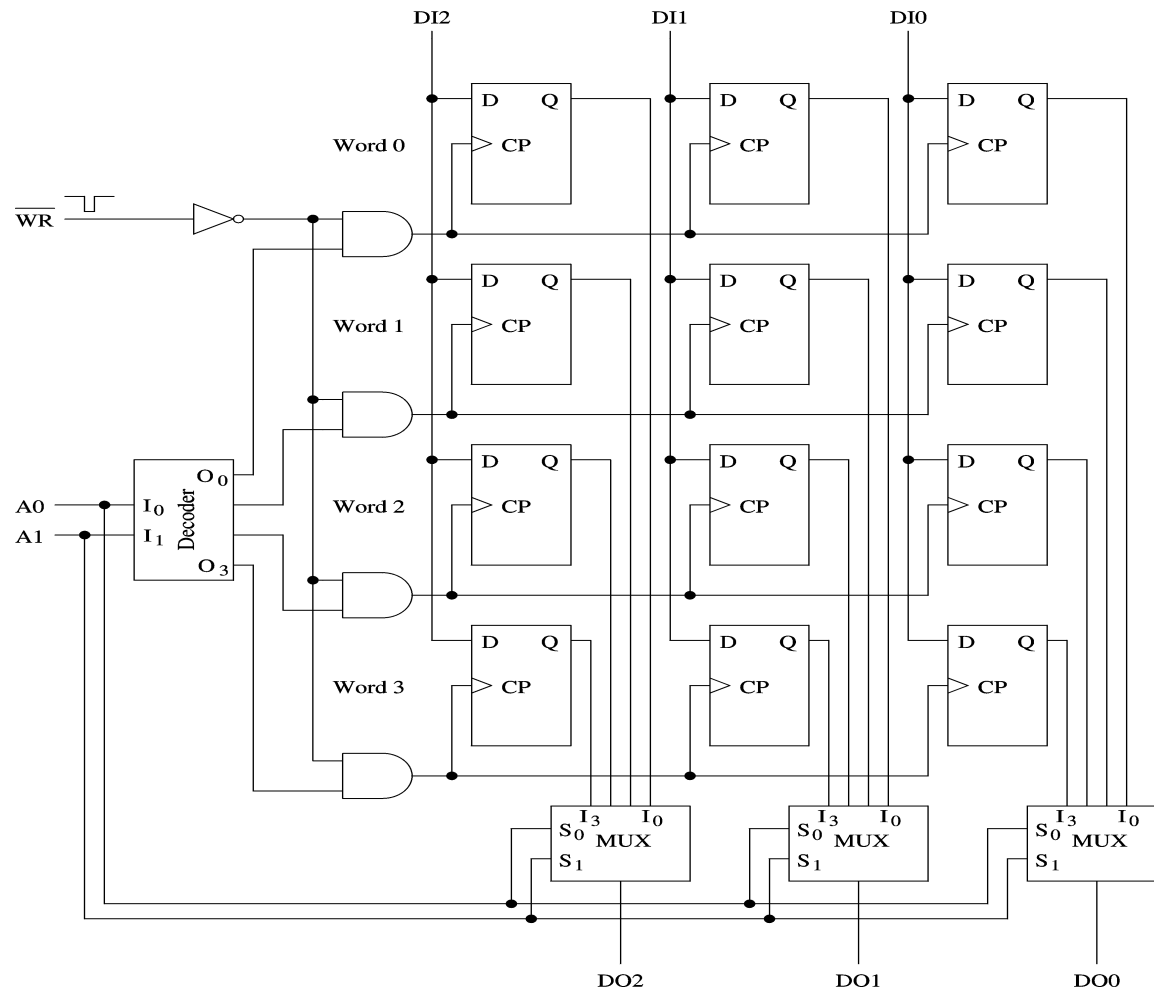
# Memory Design with D Flip Flops (cont'd)



# Memory Design with D Flip Flops (cont'd)

---

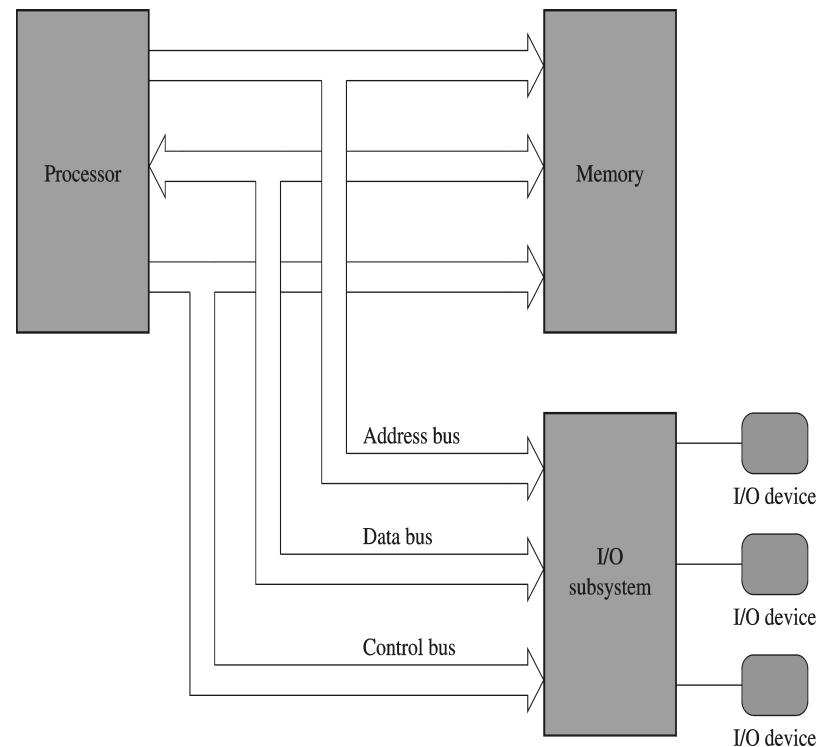- Problems with the design
  - \* Requires separate data in and out lines
    - » Cannot use the bidirectional data bus
  - \* Cannot use this design as a building block to design larger memories
    - » To do this, we need a chip select input
- We need techniques to connect multiple devices to a bus






# Techniques to Connect to a Bus

---

- Three techniques
  - \* Use multiplexers
    - » Example
      - We used multiplexers in the last memory design
    - » We cannot use MUXs to support bidirectional buses
  - \* Use open collector outputs
    - » Special devices that facilitate connection of several outputs *together*
  - \* Use tri-state buffers
    - » Most commonly used devices

# Techniques to Connect to a Bus (cont'd)

## Open collector technique

   


(a) Connection diagram

I2	I1	I0	Out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

(b) Truth table



 
# Techniques to Connect to a Bus (cont'd)



(a) Connection diagram

Open collector register chip

 

(b) Logic symbol

$\overline{\text{WE}}$	WA1	WA0	D inputs to
0	0	0	Word 0
0	0	1	Word 1
0	1	0	Word 2
0	1	1	Word 3
1	X	X	None


(c) Write function table

$\overline{\text{RE}}$	RA1	RA0	Output from
0	0	0	Word 0
0	0	1	Word 1
0	1	0	Word 2
0	1	1	Word 3
1	X	X	None (Z)

(d) Read function table

# Techniques to Connect to a Bus (cont'd)


## Tri-State Buffers

 

(a)



(b)  $E = 0$

 


(c)  $E = 1$

Inputs		Output DO
E	DI	
1	0	0
1	1	1
0	X	Z


(d)

# Techniques to Connect to a Bus (cont'd)

## Two example tri-state buffer chips

 


74367

 


74368
 
# Techniques to Connect to a Bus (cont'd)



8-bit tri-state register

 


(a) Connection diagram

(b) Logic symbol

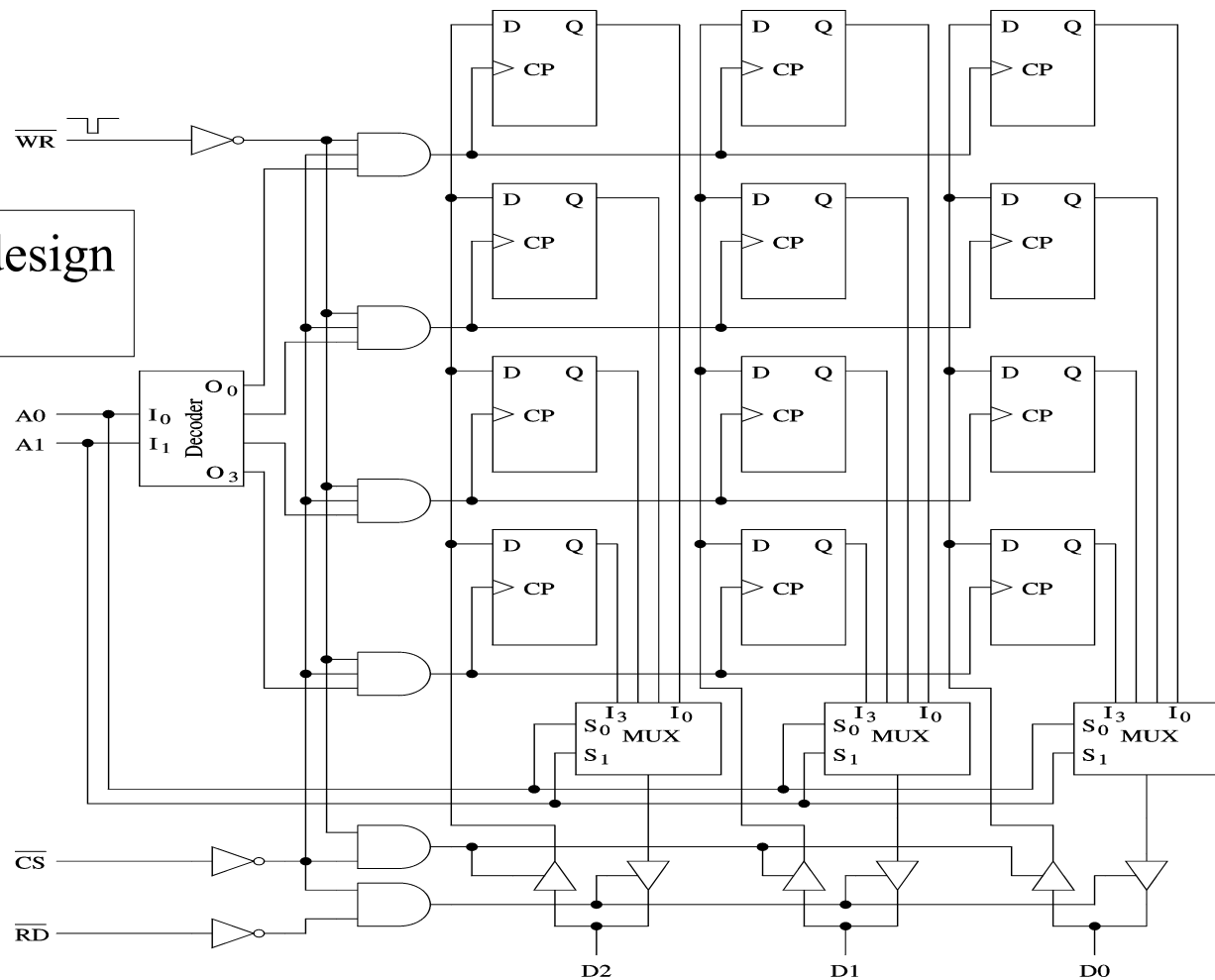
# Building a Memory Block

A 4 X 3 memory design  
using D flip-flops




## Building a Memory Block (cont'd)
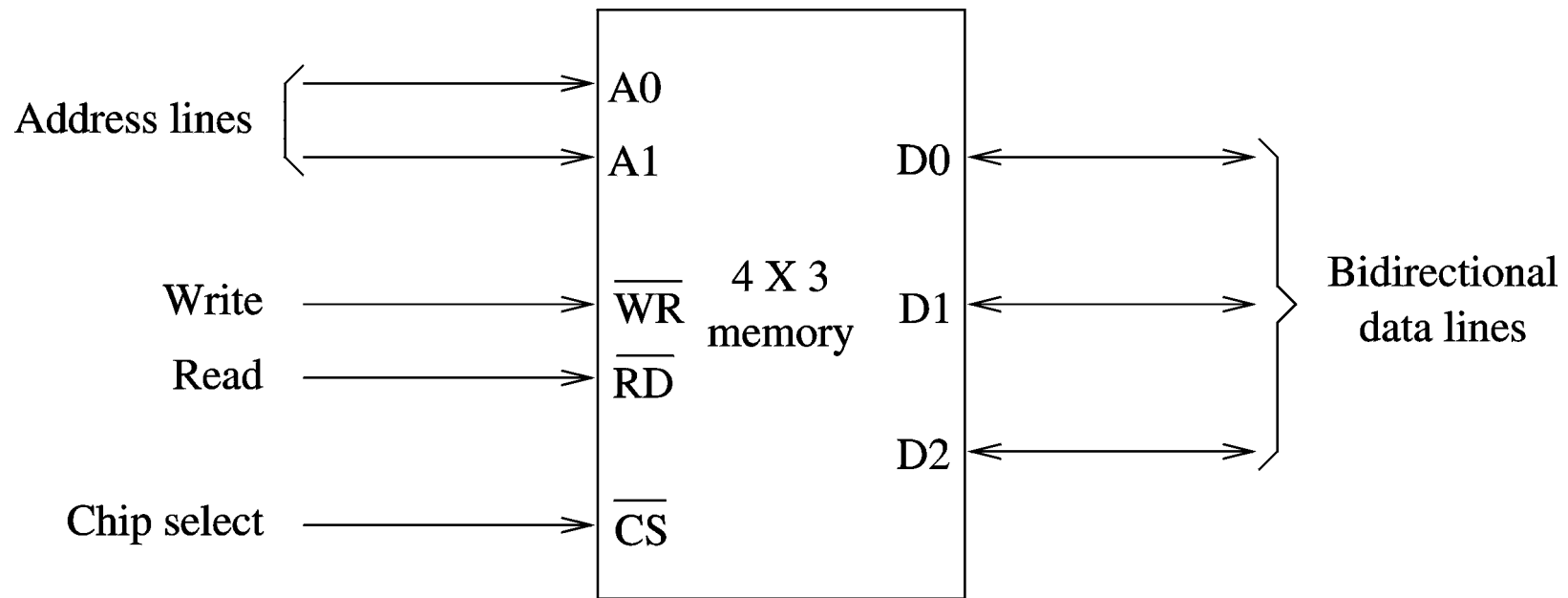
### Block diagram representation of a 4x3 memory



# Building Larger Memories

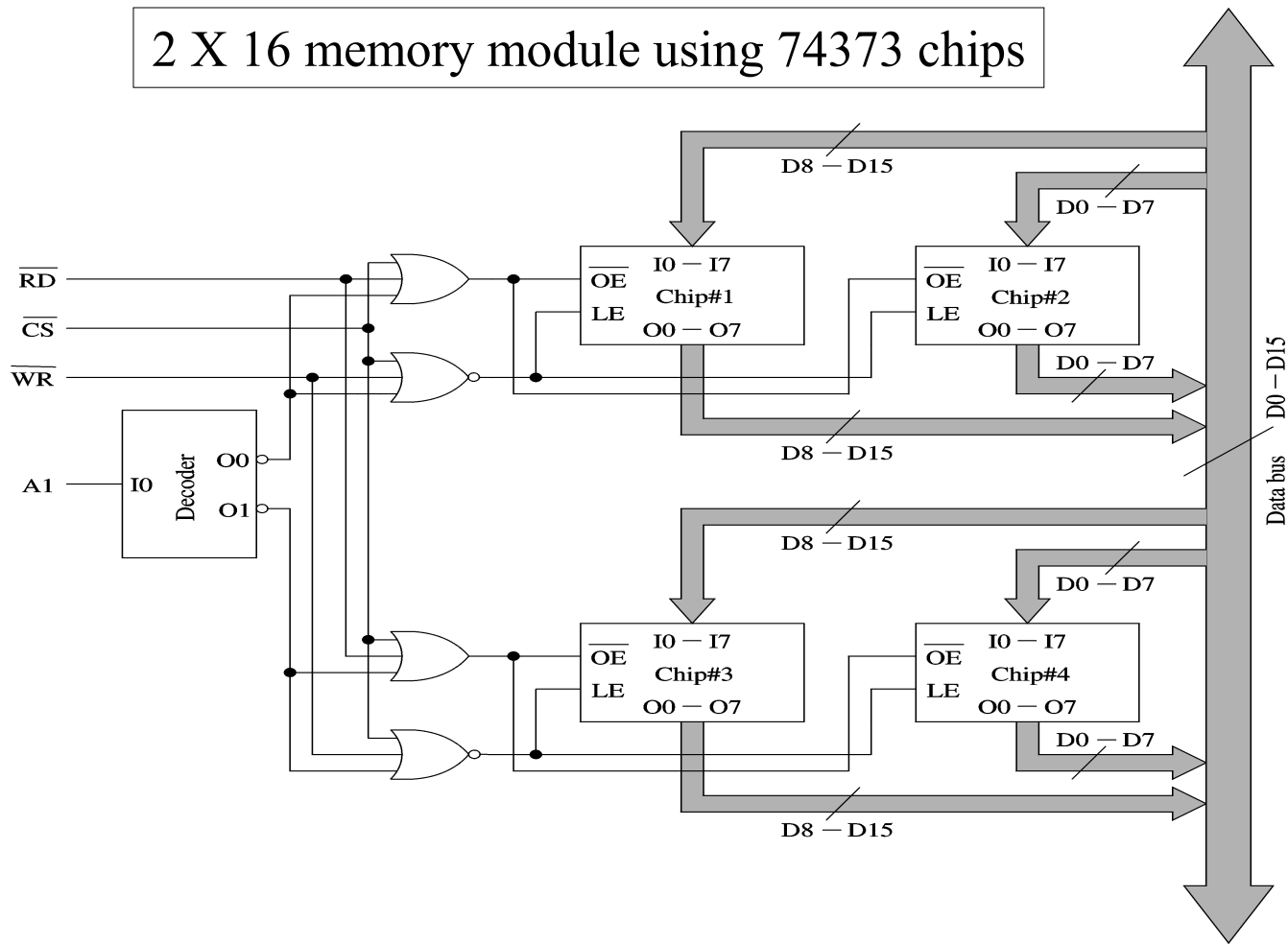

# Designing Larger Memories


---

- Issues involved
  - \* Selection of a memory chip
    - » Example: To design a 64M X 32 memory, we could use
      - Eight 64M X 4 in 1 X 8 array (i.e., single row)
      - Eight 32M X 8 in 2 X 4 array
      - Eight 16M X 16 in 4 X 2 array
- Designing M X N memory with D X W chips
  - \* Number of chips =  $M \cdot N / D \cdot W$
  - \* Number of rows =  $M / D$
  - \* Number of columns =  $N / W$



# Designing Larger Memories (cont'd)


64M X 32  
memory using  
16M X 16 chips

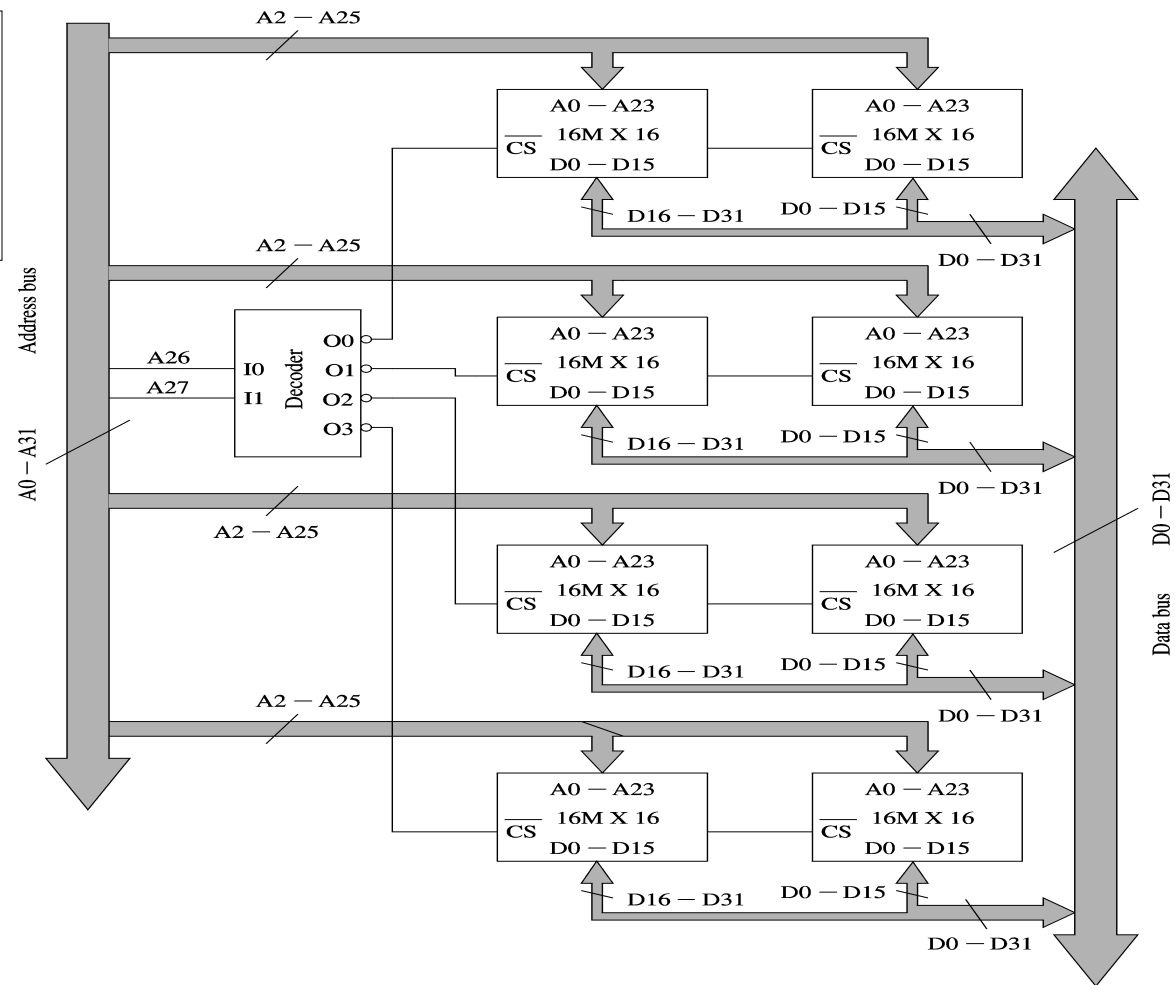
 
## Designing Larger Memories (cont'd)


---

- Design is simplified by partitioning the address lines (M X N memory with D X W memory chips)
  - \* Z bits are not connected ( $Z = \log_2(N/8)$ )
  - \* Y bits are connected to all chips ( $Y = \log_2 D$ )
  - \* X remaining bits are used to map the memory block
    - » Used to generate chip selects




# Memory Mapping

## Full mapping

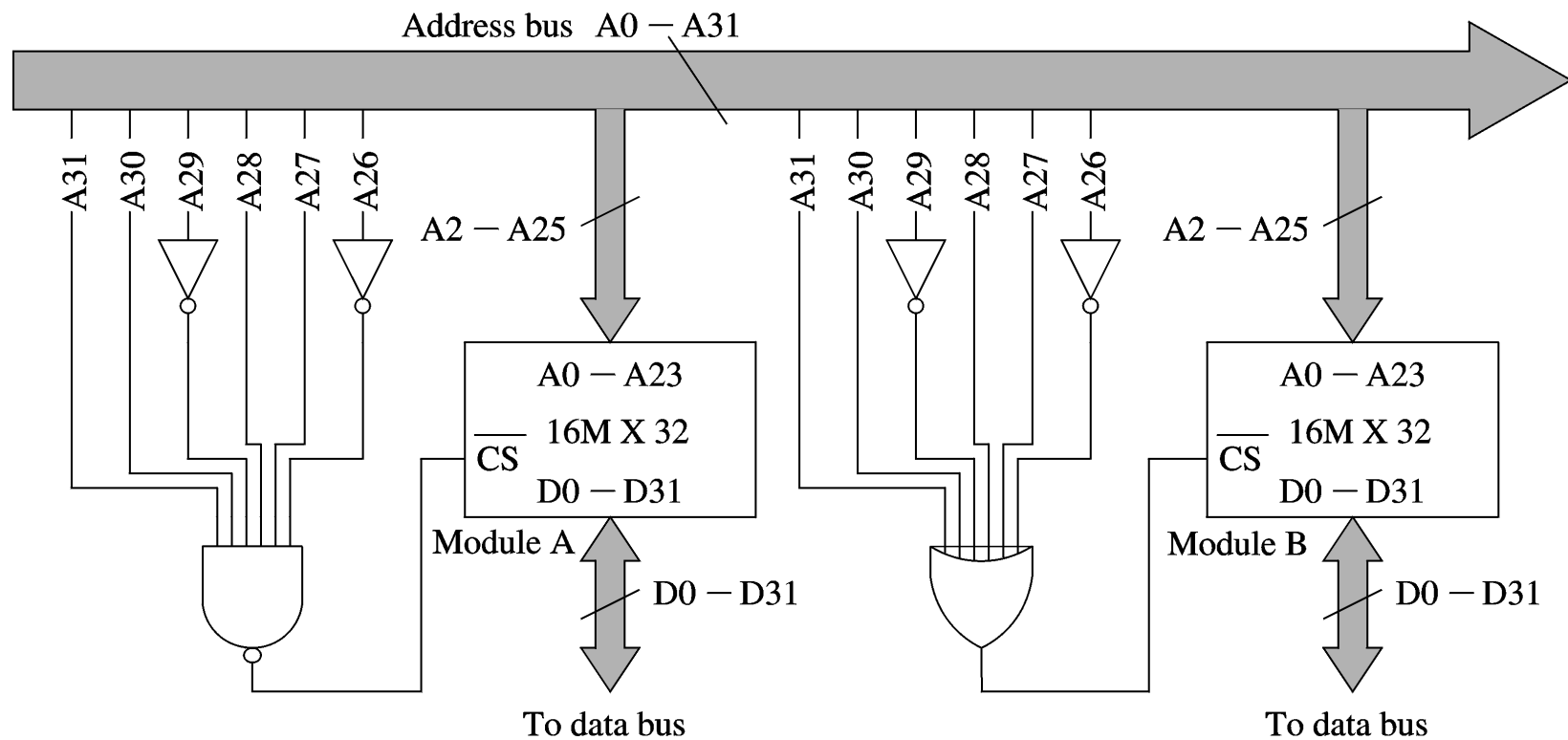


# Memory Mapping (cont'd)

## Partial mapping

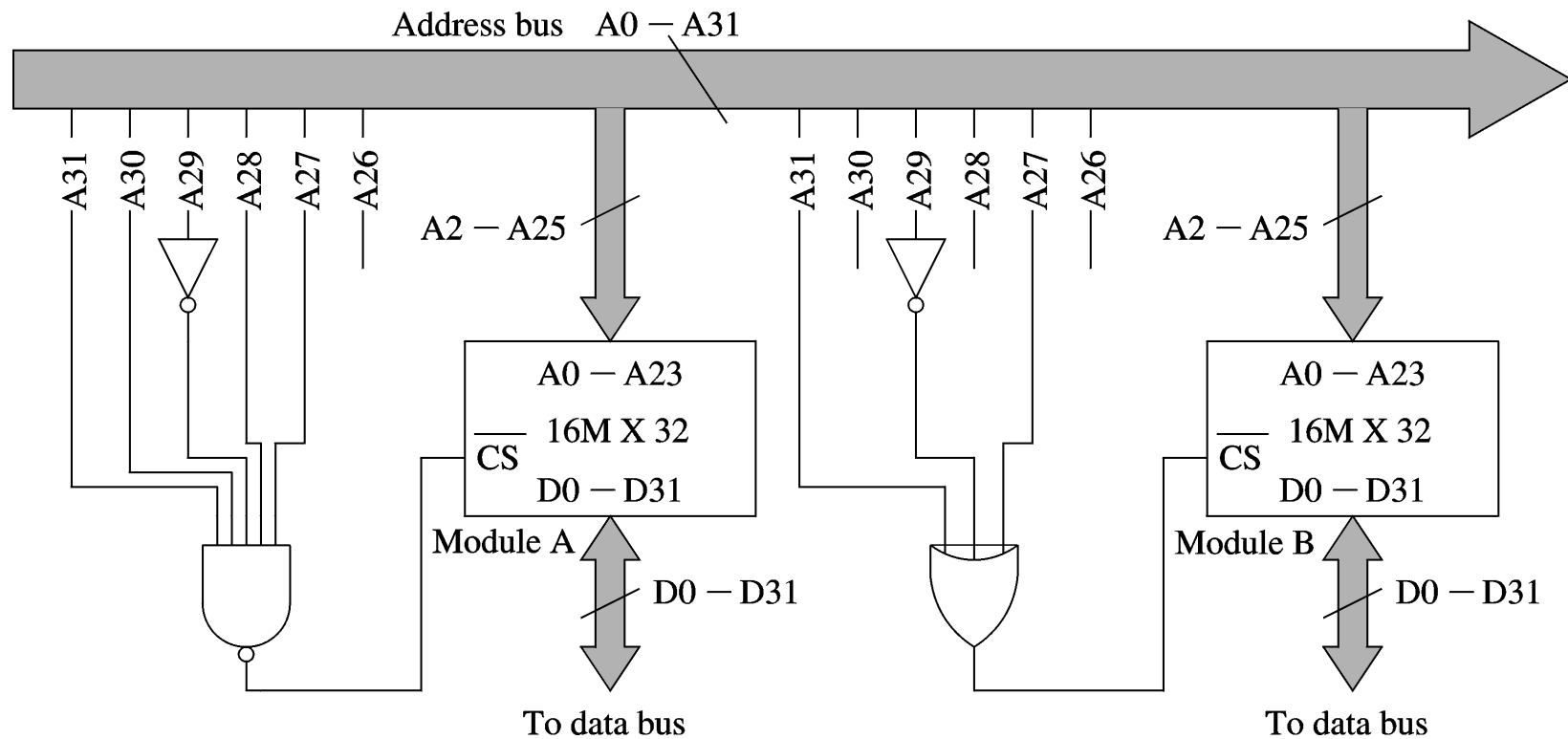

# Alignment of Data

 

# Alignment of Data (cont'd)

---

- Alignment
  - \* 2-byte data: Even address
    - » Rightmost address bit should be zero
  - \* 4-byte data: Address that is multiple of 4
    - » Rightmost 2 bits should be zero
  - \* 8-byte data: Address that is multiple of 8
    - » Rightmost 3 bits should be zero
  - \* Soft alignment
    - » Can handle aligned as well as unaligned data
  - \* Hard alignment
    - » Handles only aligned data (enforces alignment)

# Interleaved Memory

---

- In our memory designs
  - \* Block of contiguous memory addresses is mapped to a module
    - » One advantage
      - Incremental expansion
    - » Disadvantage
      - Successive accesses take more time
        - Not possible to hide memory latency
- Interleaved memories
  - \* Improve access performance
    - » Allow overlapped memory access
    - » Use multiple banks and access all banks simultaneously
      - Addresses are spread over banks
        - Not mapped to a single memory module

## Interleaved Memory (cont'd)

---


- The  $n$ -bit address is divided into two  $r$  and  $m$  bits:

$$n = r + m$$


- Normal memory
  - \* Higher order  $r$  bits identify a module
  - \* Lower order  $m$  bits identify a location in the module
    - » Called high-order interleaving
- Interleaved memory
  - \* Lower order  $r$  bits identify a module
  - \* Higher order  $m$  bits identify a location in the module
    - » Called low-order interleaving
  - \* Memory modules are referred to as memory banks



## Interleaved Memory (cont'd)

 

(a) Normal memory address mapping

 

(b) Interleaved memory address mapping


## Interleaved Memory (cont'd)

---


- Two possible implementations
  - \* Synchronized access organization
    - » Upper  $m$  bits are presented to all banks simultaneously
    - » Data are latched into output registers (MDR)
    - » During the data transfer, next  $m$  bits are presented to initiate the next cycle
  - \* Independent access organization
    - » Synchronized design does not efficiently support access to non-sequential access patterns
    - » Allows pipelined access even for arbitrary addresses
    - » Each memory bank has a memory address register (MAR)
      - No need for MDR

# Interleaved Memory (cont'd)


## Synchronized access organization

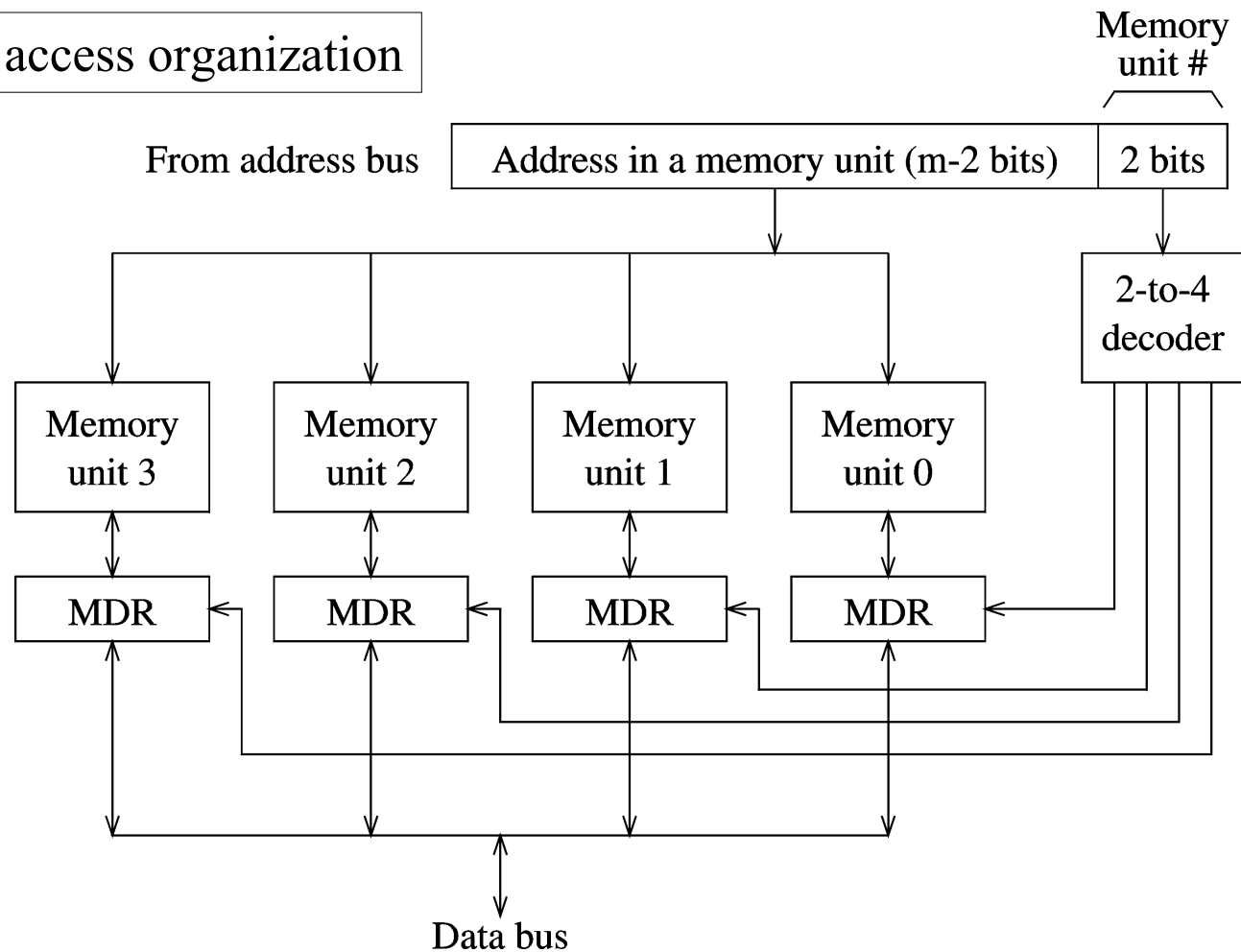

# Interleaved Memory (cont'd)

 

(a) Noninterleaved memory access

 


(b) Interleaved memory access

Interleaved memory allows pipelined access to memory

# Interleaved Memory (cont'd)

## Independent access organization

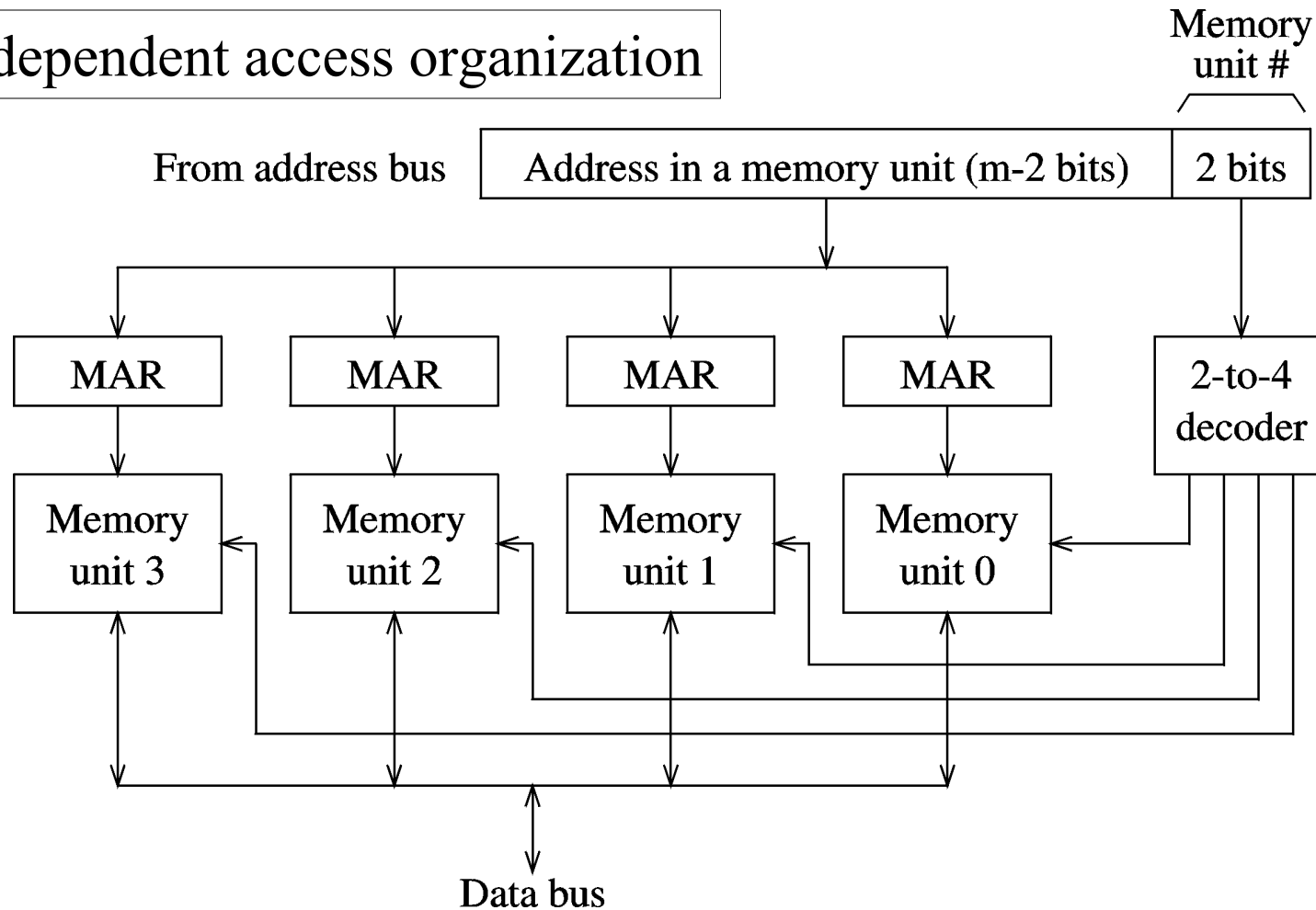

## Interleaved Memory (cont'd)

---

- Number of banks
  - \*  $M$  = memory access time in cycles
  - \* To provide one word per cycle
    - » Number of banks  $\geq M$
- Drawbacks of interleaved memory
  - \* Involves complex design
    - » Example: Need MDR or MAR
  - \* Reduced fault-tolerance
    - » One bank failure leads to failure of the whole memory
  - \* Cannot be expanded incrementally

---

Last slide