
Sequential Circuits

Chapter 4

S. Dandamudi

Outline


- Introduction
- Clock signal
 - * Propagation delay
- Latches
 - * SR latch
 - * Clocked SR latch
 - * D latch
 - * JK latch
- Flip flops
 - * D flip flop
 - * JK flip flop
- Example chips
- Example sequential circuits
 - * Shift registers
 - * Counters
- Sequential circuit design
 - * Simple design examples
 - » Binary counter
 - » General counter
 - * General design process
 - » Examples
 - Even-parity checker
 - Pattern recognition

Introduction

- Output depends on current as well as past inputs
 - * Depends on the history
 - * Have “memory” property
- Sequential circuit consists of
 - » Combinational circuit
 - » Feedback circuit
 - * Past input is encoded into a set of state variables
 - » Uses feedback (to feed the state variables)
 - Simple feedback
 - Uses flip flops


Introduction (cont'd)

Main components of a sequential circuit

 


Introduction (cont'd)

 - Feedback circuit can be
 - * A simple interconnection some outputs to input, or
 - * A combinational circuit with “memory” property
 - » Uses flip-flops we discuss later
- Feedback can potentially introduce instability



(a) Stable circuit

 


(b) Unstable circuit


Clock Signal

- Digital circuits can be operated in
 - * Asynchronous mode
 - » Circuits operate independently
 - Several disadvantages
 - * Synchronous mode
 - » Circuits operate in lock-step
 - » A common clock signal drives the circuits
- Clock signal
 - * A sequence of 1s and 0s (ON and OFF periods)
 - * Need not be symmetric


Clock Signal (cont'd)

 

(a) Symmetric

 

(b) Smaller ON period

 


(c) Smaller OFF period


Clock Signal (cont'd)

- Clock serves two distinct purposes
 - * Synchronization point
 - » Start of a cycle
 - » End of a cycle
 - » Intermediate point at which the clock signal changes levels
 - * Timing information
 - » Clock period, ON, and OFF periods
- Propagation delay
 - * Time required for the output to react to changes in the inputs

Clock Signal (cont'd)

 

(a) Circuit diagram

 


(b) Timing diagram


Latches

- Can remember a bit
- Level-sensitive (not edge-sensitive)

A NOR gate implementation of SR latch

 

(a) Circuit diagram

 


(b) Logic symbol

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	0

 
(c) Truth table

Latches (cont'd)

- SR latch outputs follow inputs
- In clocked SR latch, outputs respond at specific instances
 - * Uses a clock signal




(a) Circuit diagram

 

 
(b) Logic symbol

Latches (cont'd)

- D Latch
 - * Avoids the $SR = 11$ state



(a) Circuit diagram

 

(b) Logic symbol


D	Q_{n+1}
0	0
1	1

(c) Truth table


Flip-Flops

- Edge-sensitive devices
 - * Changes occur either at positive or negative edges

Positive edge-triggered D flip-flop

 

(a) Circuit diagram

 


(b) Logic symbol

Flip-Flops (cont'd)

- Notation

- * Not strictly followed in the literature

 
- » We follow the following notation for latches and flip-flops




Flip-Flops (cont'd)

JK flip-flop
(master-slave)


J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

 

(a) Circuit diagram

 

(b) Logic symbol

 


(c) Timing diagram

Flip-Flops (cont'd)


Two example chips

D latches

 

(a) 7477

JK flip-flops

 


(b) 7476

 Example Sequential Circuits


- Shift Registers
 - * Can shift data left or right with each clock pulse

A 4-bit shift register using JK flip-flops




Example Sequential Circuits (cont'd)

74164 shift
Register chip

 

(a) Connection diagram

 


(b) Logic diagram

Example Sequential Circuits (cont'd)


- Counters
 - * Easy to build using JK flip-flops
 - » Use the JK = 11 to toggle
 - * Binary counters
 - » Simple design
 - B bits can count from 0 to 2^B-1
 - » Ripple counter
 - Increased delay as in ripple-carry adders
 - Delay proportional to the number of bits
 - » Synchronous counters
 - Output changes more or less simultaneously
 - Additional cost/complexity

Example Sequential Circuits (cont'd)

 


A modulo-8
binary ripple
counter

(a) Circuit diagram

 


(b) Timing diagram


Example Sequential Circuits (cont'd)

 


(a) Connection diagram

 

(b) Logic symbol

 

(c) State diagram of 74161

 

(d) State diagram of 74160

Example Sequential Circuits (cont'd)

Function table


H = high

L = low

X = don't care

$\overline{\text{MR}}$	$\overline{\text{PE}}$	CET	CEP	Action on clock rising edge
L	X	X	X	Clear
H	L	X	X	Parallel load ($P_n \rightarrow Q_n$)
H	H	H	H	Count (increment)
H	H	L	X	No change (hold); TC is low
H	H	X	L	No change (hold)

Example Sequential Circuits (cont'd)

 

Sequential Circuit Design

- Sequential circuit consists of
 - * A combinational circuit that produces output
 - * A feedback circuit
 - » We use JK flip-flops for the feedback circuit
- Simple counter examples using JK flip-flops
 - * Provides alternative counter designs
 - * We know the output
 - » Need to know the input combination that produces this output
 - » Use an excitation table
 - Built from the truth table

Sequential Circuit Design (cont'd)

(a) JK flip-flop truth table

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b) Excitation table for JK flip-flops

Q_n	Q_{n+1}	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

Sequential Circuit Design (cont'd)

- Build a design table that consists of
 - * Current state output
 - * Next state output
 - * JK inputs for each flip-flop
- Binary counter example
 - * 3-bit binary counter
 - * 3 JK flip-flops are needed
 - * Current state and next state outputs are 3 bits each
 - * 3 pairs of JK inputs

Sequential Circuit Design (cont'd)

Design table for the binary counter example

Present state			Next state			JK flip-flop inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	d	0	d	1	d
0	0	1	0	1	0	0	d	1	d	d	1
0	1	0	0	1	1	0	d	d	0	1	d
0	1	1	1	0	0	1	d	d	1	d	1
1	0	0	1	0	1	d	0	0	d	1	d
1	0	1	1	1	0	d	0	1	d	d	1
1	1	0	1	1	1	d	0	d	0	1	d
1	1	1	0	0	0	d	1	d	1	d	1

Sequential Circuit Design (cont'd)

Use K-maps to simplify expressions for JK inputs

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	d	d	d	d

$$J_A = B C$$

		BC			
		00	01	11	10
A	0	d	d	d	d
	1	0	0	1	0

$$K_A = B C$$

		BC			
		00	01	11	10
A	0	0	1	d	d
	1	0	1	d	d

$$J_B = C$$

		BC			
		00	01	11	10
A	0	d	d	1	0
	1	d	d	1	0

$$K_B = C$$

		BC			
		00	01	11	10
A	0	1	d	d	1
	1	1	d	d	1


$$J_C = 1$$

		BC			
		00	01	11	10
A	0	d	1	1	d
	1	d	1	1	d

$$K_C = 1$$

Sequential Circuit Design (cont'd)

 - Final circuit for the binary counter example
 - * Compare this design with the synchronous counter design




Sequential Circuit Design (cont'd)

- A more general counter design
 - * Does not step in sequence

$0 \rightarrow 3 \rightarrow 5 \rightarrow 7 \rightarrow 6 \rightarrow 0$

 - Same design process
- One significant change
 - * Missing states
 - » 1, 2, and 4
 - » Use don't cares for these states



Sequential Circuit Design (cont'd)

Design table for the general counter example

Present state			Next state			JK flip-flop inputs					
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	1	1	0	d	1	d	1	d
0	0	1	—	—	—	d	d	d	d	d	d
0	1	0	—	—	—	d	d	d	d	d	d
0	1	1	1	0	1	1	d	d	1	d	0
1	0	0	—	—	—	d	d	d	d	d	d
1	0	1	1	1	1	d	0	1	d	d	0
1	1	0	0	0	0	d	1	d	1	0	d
1	1	1	1	1	0	d	0	d	0	d	1

Sequential Circuit Design (cont'd)

K-maps to
simplify
JK input
expressions

		BC			
		00	01	11	10
A	0	0	d	1	d
	1	d	d	d	d

$$J_A = B$$

		BC			
		00	01	11	10
A	0	d	d	d	d
	1	d	0	0	1

$$K_A = \bar{C}$$

		BC			
		00	01	11	10
A	0	1	d	d	d
	1	d	1	d	d

$$J_B = 1$$

		BC			
		00	01	11	10
A	0	d	d	1	d
	1	d	d	0	1

$$K_B = \bar{A} + \bar{C}$$

		BC			
		00	01	11	10
A	0	1	d	d	d
	1	d	d	d	0


$$J_C = \bar{A}$$

		BC			
		00	01	11	10
A	0	d	d	0	d
	1	d	0	1	d

$$K_C = A B$$

Sequential Circuit Design (cont'd)

 Final circuit for the general counter example




General Design Process

- FSM can be used to express the behavior of a sequential circuit
 - » Counters are a special case
 - * State transitions are indicated by arrows with labels X/Y
 - » X: inputs that cause system state change
 - » Y: output generated while moving to the next state
- Look at two examples
 - * Even-parity checker
 - * Pattern recognition

General Design Process (cont'd)

 - Even-parity checker
 - * FSM needs to remember one of two facts
 - » Number of 1's is odd or even
 - » Need only two states
 - 0 input does not change the state
 - 1 input changes state
 - * Simple example
 - » Complete the design as an exercise




General Design Process (cont'd)

- Pattern recognition example
 - * Outputs 1 whenever the input bit sequence has exactly two 0s in the last three input bits
 - * FSM requires three special states to during the initial phase
 - » S0 – S2
 - * After that we need four states
 - » S3: last two bits are 11
 - » S4: last two bits are 01
 - » S5: last two bits are 10
 - » S6: last two bits are 00

General Design Process (cont'd)

 State diagram
for the pattern
recognition
example



General Design Process (cont'd)

- Steps in the design process
 1. Derive FSM
 2. State assignment
 - * Assign flip-flop states to the FSM states
 - * Necessary to get an efficient design
 3. Design table derivation
 - * Derive a design table corresponding to the assignment in the last step
 4. Logical expression derivation
 - * Use K-maps as in our previous examples
 5. Implementation

General Design Process (cont'd)

- State assignment
 - * Three heuristics
 - » Assign adjacent states for
 - states that have the same next state
 - states that are the next states of the same state
 - States that have the same output for a given input
 - * For our example
 - » Heuristic 1 groupings: (S1, S3, S5)² (S2, S4, S6)²
 - » Heuristic 2 groupings: (S1, S2) (S3, S4)³ (S5, S6)³
 - » Heuristic 1 groupings: (S4, S5)

General Design Process (cont'd)

State table for
the pattern
recognition
example

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
S0	S2	S1	0	0
S1	S4	S3	0	0
S2	S6	S5	0	0
S3	S4	S3	0	0
S4	S6	S5	1	0
S5	S4	S3	1	0
S6	S6	S5	0	1

General Design Process (cont'd)

K-map for state assignment

		BC			
		00	01	11	10
A	0	S0	S3	S5	S1
	1		S4	S6	S2

State assignment

State		A	B	C
S0	=	0	0	0
S1	=	0	1	0
S2	=	1	1	0
S3	=	0	0	1
S4	=	1	0	1
S5	=	0	1	1
S6	=	1	1	1

General Design Process (cont'd)

Design
table

Present state			Present state	Next state			Present state	JK flip-flop inputs					
A	B	C	X	A	B	C	Y	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	1	1	0	0	1	d	1	d	0	d
0	0	0	1	0	1	0	0	0	d	1	d	0	d
0	0	1	0	1	0	1	0	1	d	0	d	d	0
0	0	1	1	0	0	1	0	0	d	0	d	d	0
0	1	0	0	1	0	1	0	1	d	d	1	1	d
0	1	0	1	0	0	1	0	0	d	d	1	1	d
0	1	1	0	1	0	1	1	1	d	d	1	d	0
0	1	1	1	0	0	1	0	0	d	d	1	d	0
1	0	1	0	1	1	1	1	1	0	1	d	d	0
1	0	1	1	0	1	1	0	d	1	1	d	d	0
1	1	0	0	1	1	1	0	d	0	d	0	1	d
1	1	0	1	0	1	1	0	d	1	d	0	1	d
1	1	1	0	1	1	1	0	d	0	d	0	d	0
1	1	1	1	0	1	1	1	d	1	d	0	d	0

General Design Process (cont'd)

		CX			
AB		00	01	11	10
00		1	0	0	1
01		1	0	0	1
11		d	d	d	d
10		d	d	d	d

$$J_A = \bar{X}$$

		CX			
AB		00	01	11	10
00		d	d	d	d
01		d	d	d	d
11		0	1	1	0
10		d	d	1	0

$$K_A = X$$

K-maps for JK inputs

		CX			
AB		00	01	11	10
00		1	1	0	0
01		d	d	d	d
11		d	d	d	d
10		d	d	1	1

$$J_B = \bar{C} + A$$

		CX			
AB		00	01	11	10
00		d	d	d	d
01		1	1	1	1
11		0	0	0	0
10		d	d	d	d

$$K_B = \bar{A}$$

K-map for the output

		CX			
AB		00	01	11	10
00		0	0	d	d
01		1	1	d	d
11		1	1	d	d
10		d	d	d	d

$$J_C = B$$


		CX			
AB		00	01	11	10
00		d	d	0	0
01		d	d	0	0
11		d	d	0	0
10		d	d	0	0

$$K_C = 0$$

		CX			
AB		00	01	11	10
00		0	0	0	0
01		0	0	0	1
11		0	0	1	0
10		d	d	0	1


$$Y = \bar{A} B C \bar{X} + A B C X + A \bar{B} \bar{X}$$

General Design Process (cont'd)

 

(a)

Final implementation

 

(b)

Summary

- Output of a sequential circuit
 - * Depends on the current input, and
 - * Past history
- Typically consists of
 - * A combinational circuit
 - * A feedback circuit
- Provides “memory” property
 - * Can be used to store a single bit of information
- Discussed sequential circuit design

Last slide